

2.

~~DMT~~


DMT

PLC + DPLC


15 ©

$$\overline{c+d}$$

b



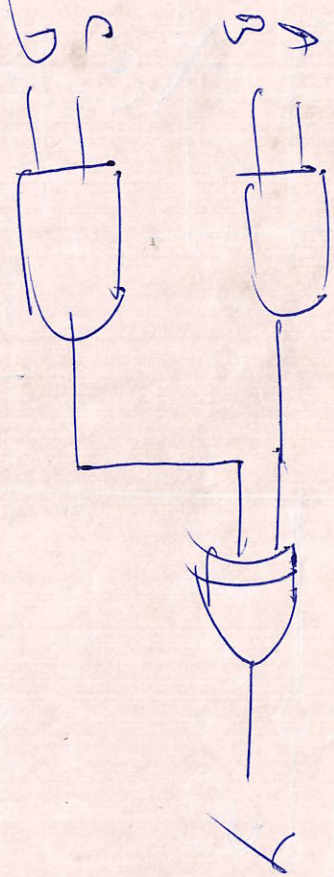


$$\overline{CD} = \overline{c+d}$$

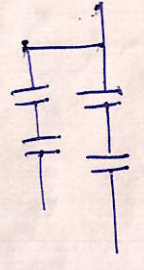


$$Y = AB + CD$$
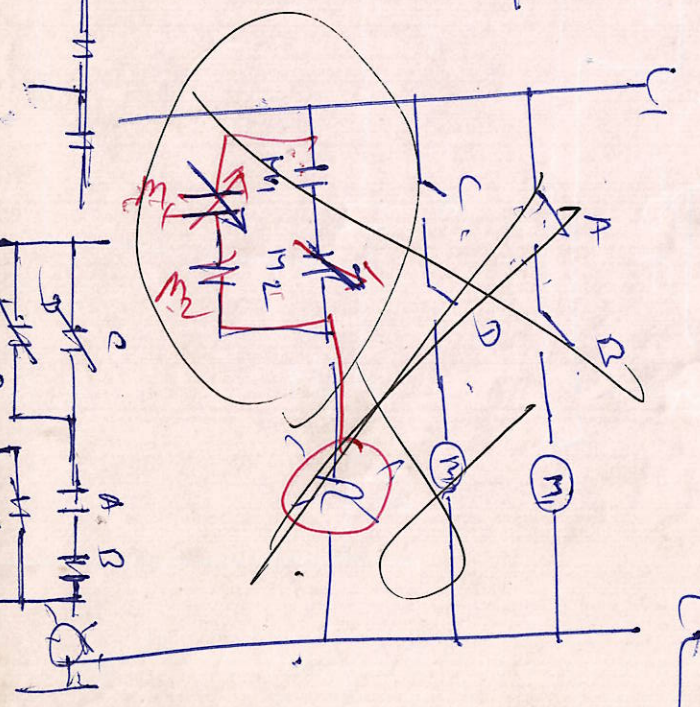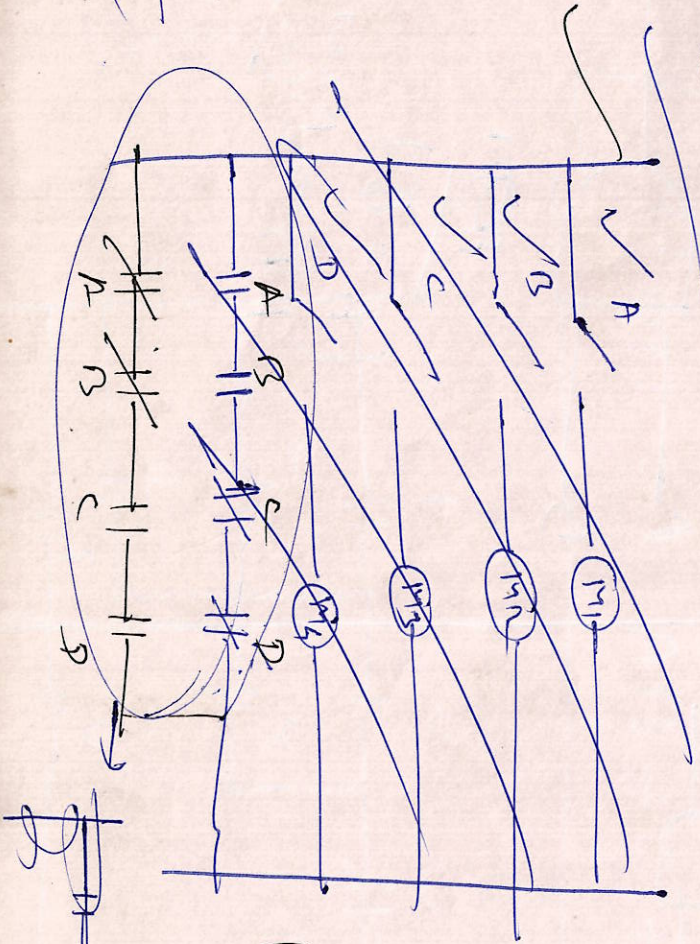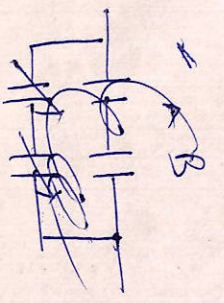
$$Y = (AB) \cdot (CD)' + (AB)' \cdot (CD)$$




16


Debye gate 21

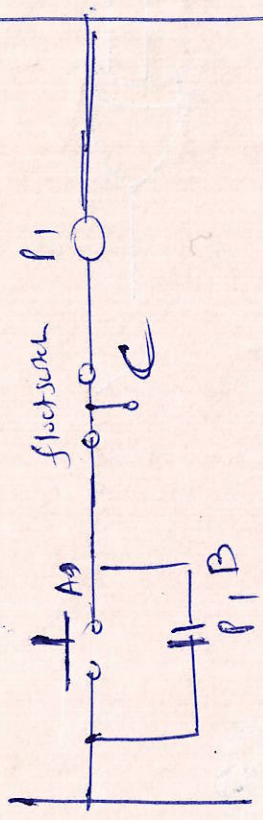

let $P_1 = (A+B) \cdot C$

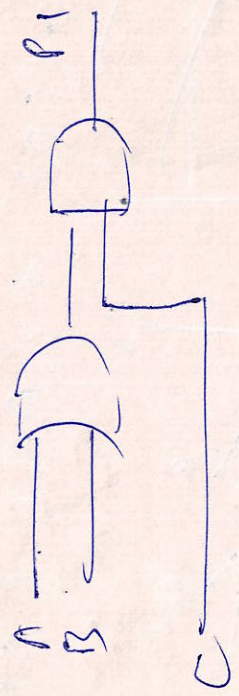

16

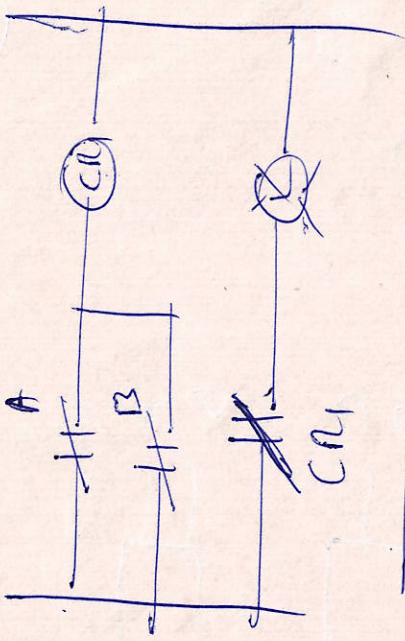

$L = \overline{(A' + B')}$

$C = A \cdot B$



$\overline{(A + B)}$
 $\overline{A \cdot B} = A + B$

(17)

$Y_{OP} = 2$

Fig A


$$Y = AB + CD + E(F + G) = (1 \cdot 2) + (3 \cdot 4) + 5 \cdot (5 + 7)$$
$$Y = AB + CD + E(F + G)$$

Fig C

$$Y_{OP} = AB + C + D + BE$$

Fig b

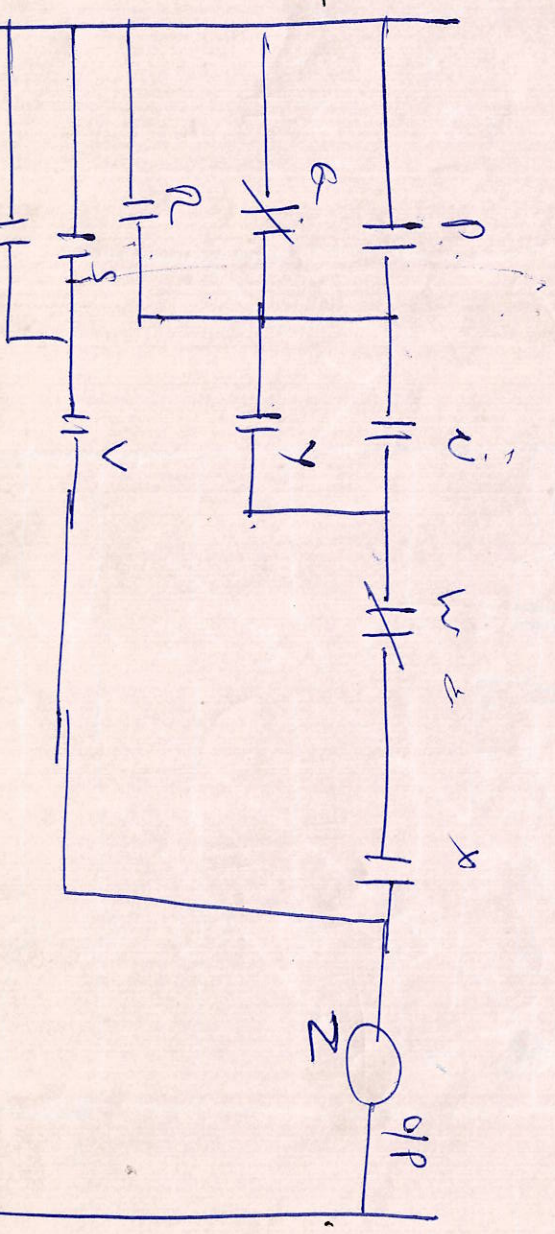
$$\left. \begin{aligned} & (P + Q + R)(U + V)(W)(X) + \\ & (Y + T)V \end{aligned} \right\}$$



Ans $Z = \{(S+T) \cdot V\}$
 i.e. if

$$Z = [(P + \bar{Q} + R) \cdot (U + V) \cdot \bar{W} \cdot X] + (S + T) \cdot V$$

Proposed Gate

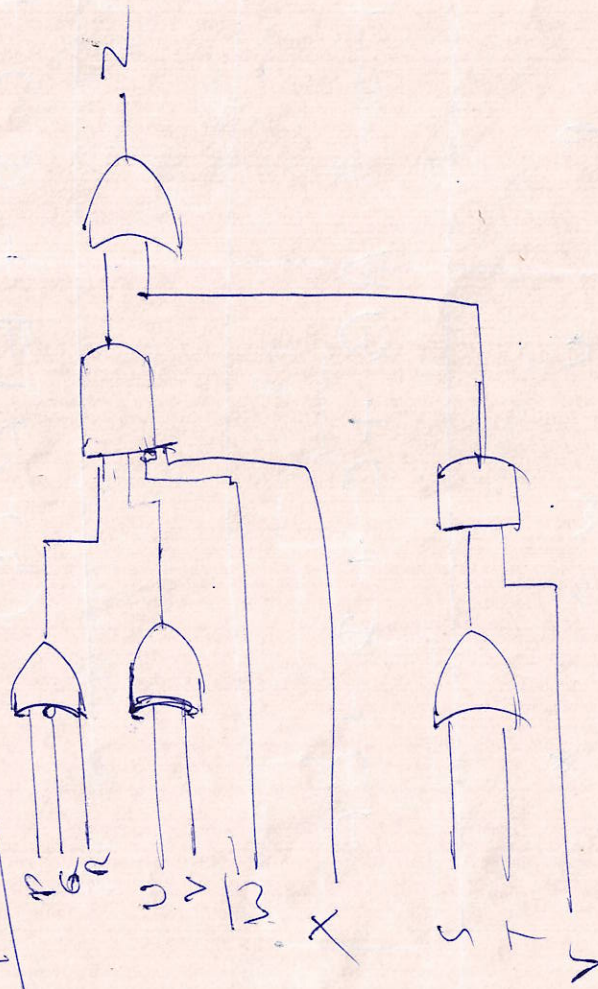

- ①
- ②
- ③
- ④
- ⑤

18
fig A

$S = \left[(L + M' + N) + (R_1) \right] \cdot R$

~~$\left[(L + M' + N) \cdot (R_1) \right] R$~~


~~$\left[(L' \cdot M \cdot N') \cdot (R_1 + R_2) \right] R$~~

~~$(L + M' + N) = (L' \cdot M \cdot N') \cdot (R_1 + R_2)$~~

Let $L + M' + N = X$
 $M' = Y$


$(L + M') \cdot N$

$= L' \cdot M \cdot N'$

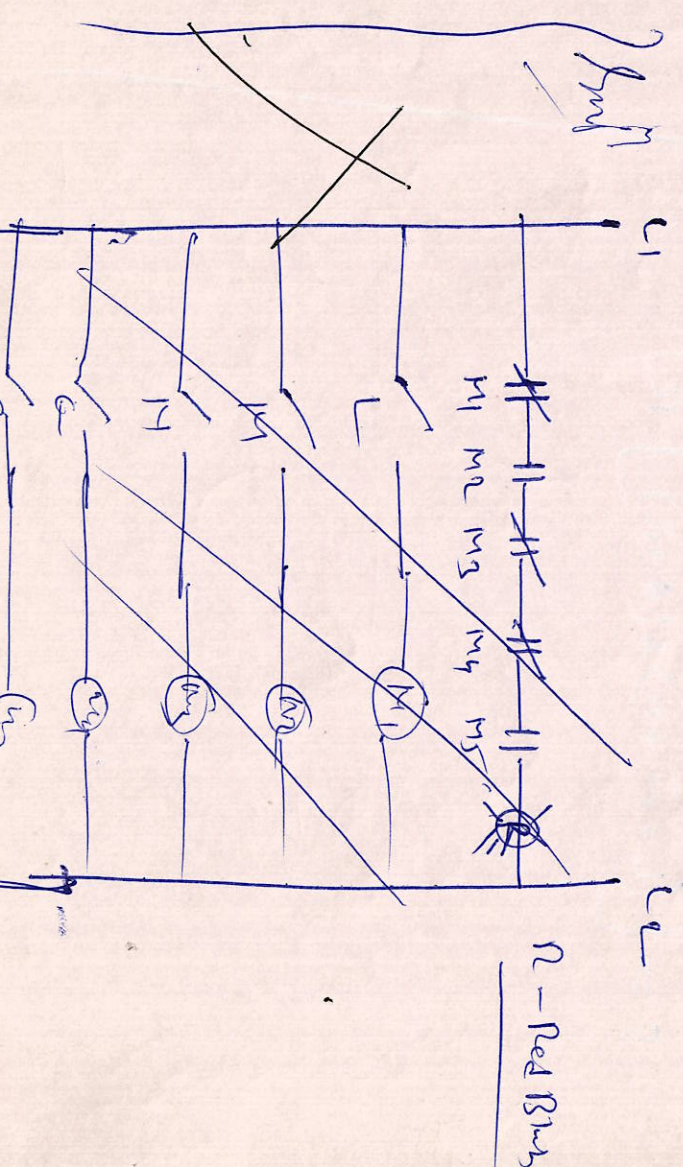

18 Aug A

PLC ladder - Pir LR

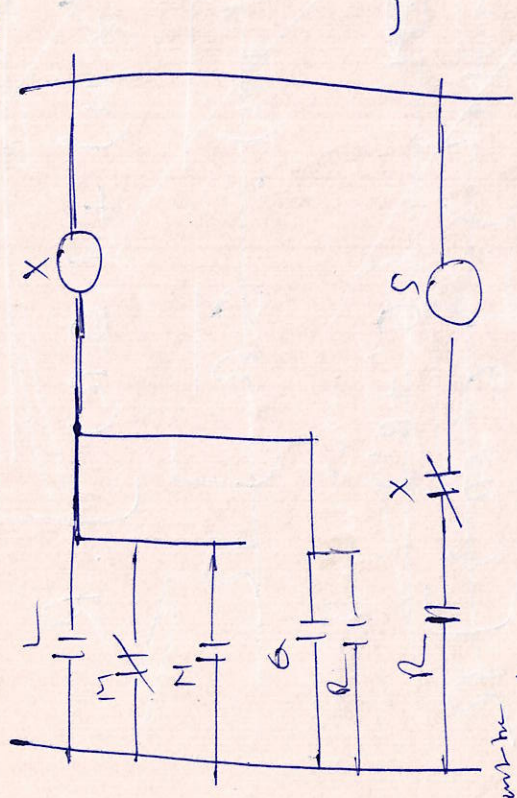


prevent the
two outputs
containing
R

Boolean Expr

$$S = [(L + \bar{M} + N) + (S + R)] R$$

- ①
- ②
- ③
- ④
- ⑤

Soln

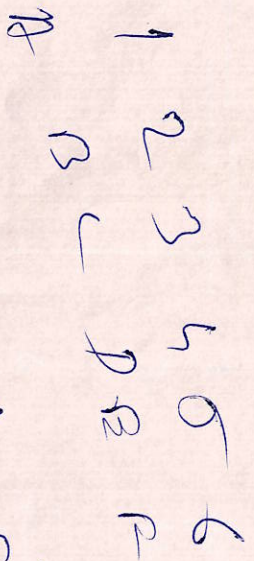


M1 to M6

opp 2

$$[(A B') + (C + D) + B]$$

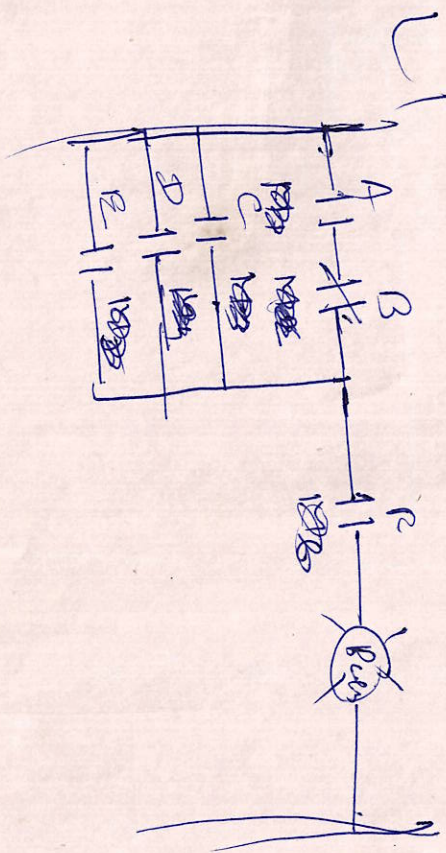
$$[\cancel{A} B' C + \cancel{C} + \cancel{D}]$$



Discrete State Process Control

Measurement

①

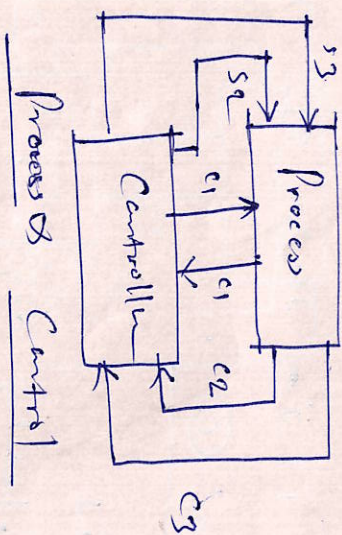

②

Refrigerator / freezer system

Fig

* The Discrete-state I/P variables are:

1. Door open / closed
2. Power switch ON/OFF
3. The frost eliminator timer
time out / refire on
4. freezer temp. high / low
5. Cooler temp. high / low
6. frost detector ON / OFF

* The discrete, 0/1 ^{state} variables are:

1. Compressor — ON/OFF
2. Light — ON/OFF
3. frost eliminator timer — started / not started
4. frost eliminator Heater/Fan — ON/OFF
5. Cooler blade — open / closed

So the total no. of events are

$$= 6 (I/P) + 5 (O/P) = 11 \text{ two state variables.}$$

∴ in 2¹¹ = 2048 possible states / events. Of course, few of these are necessary.

So the sequence of send / recd events are ⇒

① If the door is open;
the light is turn ON.

② if cooler temp is high

↓
and frat eliminator is off

then ⇒ compressor → ON

↓
cooler bottle → open
until the cooler temp is low.

③ If fratzer temp is high
and frat-eliminator is off

then ⇒ compressor → ON

↓
the fratzer temp is low.

④ frat detector is ON

↓
timer is started

↓
compressor is turning

↓
frat eliminator is turning ON

until the timer is timeout

send of 11-1

① g in 11-1 of b, c & d


② b & c in 11-1, to others

but d is in series of

either g or c.

is

Reliability diagram

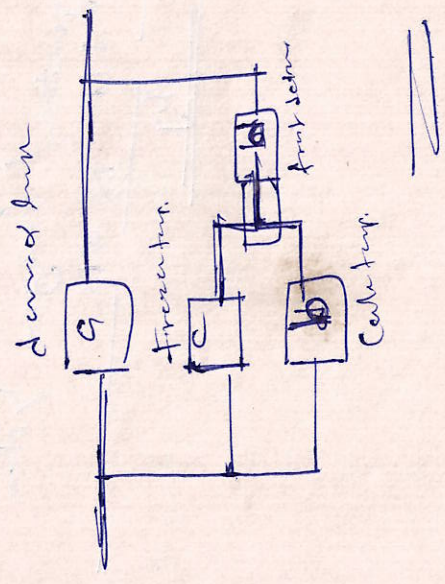


①
②
③
④
⑤

Discrete state Process Control

Definition \Rightarrow mean two states

Ex: Auto/manual
on/off
operational value

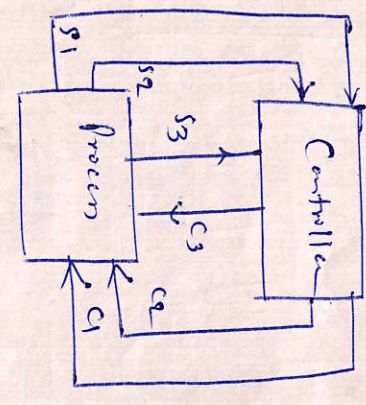

Let us, call mean of I/P variable
(s1, s2, s3) & call control o/p variables
(c1, c2, c3) of the process can
take on / be assigned only two values.

Ex:-
Motor — on/off
valve — open/closed
temp — high/low
Limit switch — closed/open & so on.

So because of each variable
Hence 6 ~~variables~~

\therefore total possible state $= 2^6 = 64$ states
out of which few will be important
& needs to consider.

Science 2) Discrete state Process Control


is a particular sequence of events
through which the process accomplished
some objective

For a simple heater

1.	Temp. L	Heater off
2.	" L	" ON
3.	" H	" OFF
4.	" H	" ON

So the system is called completely
digitized if there is only two state
at a time.

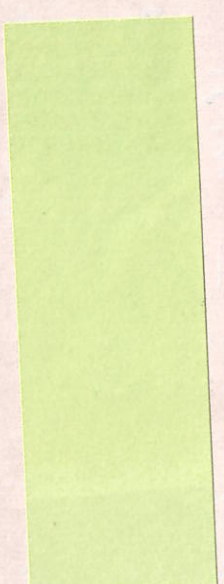Char. of the system \Rightarrow Discrete state Process
Control is called Master control system.



Unit 4 Assignments (4)

Frost-free Refrigerator/Freezer

Ans Description of the system.

- ① I/P discrete variable: → States
- I/P variable — States
1. Apply the power — ON/OFF
 2. Door — open/closed
 3. Freezer temp. — low/high
 4. Cooler temp. — low/high
 5. Frost Eliminator Timing — timeout/not timeout
 6. Frost Detector — ON/OFF

- ② O/P discrete variable: → States
- O/P variable — States
1. Frost eliminator fan — ON/OFF
 2. Frost eliminator timer — time started/not started
 3. Light — on/off
 4. cooler heater — open/closed
 5. Compressor — ON/OFF

So the total no. of (I/P + O/P) variables = 6 + 5 = 11 variables.

So total possible discrete states are $2^{11} = 2048$. out of ~~that~~ only a few of them are necessary.

"The Event Sequence are" i —


1. if Door → open, Light — ON.
2. if Cooler temp. is high & Frost eliminator is OFF, the compressor is turned on & the cooler heater is opened until the cooler temp. is low.

(C.T. → H & F.E. → OFF; Comp. → ON & C.B. open
Unit C.T. → L.)

3. if Freezer temp. → is high & Frost eliminator is OFF, the compressor is turned on & the cooler heater until the Freezer temp. comes down.

(F.T. → H & F.E. → OFF; Comp. → ON until C.T. → L.)

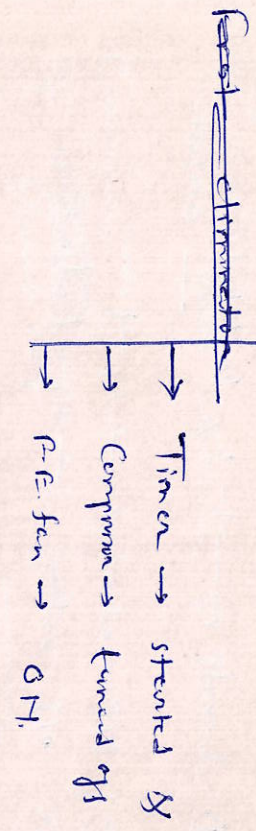
4. If the front detector is ON ~~front eliminator~~



until the front eliminator time is time out.

* Sequence of sensors & their events :-

- ① a || b, c & d.
- ② b || c
- ③ d is in series either with b or c.

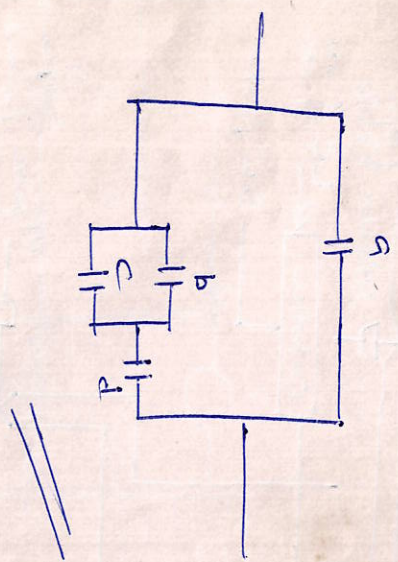

Assignment
E/P 7/8/15


Detail Approach of Discrete state variables

⑥ i.e finite set of variables = generally few state.

It is imp to be able

to distinguish between the nature of variables in a discrete state system. & these in continuous control system. To define in a better way, let us take an example =>

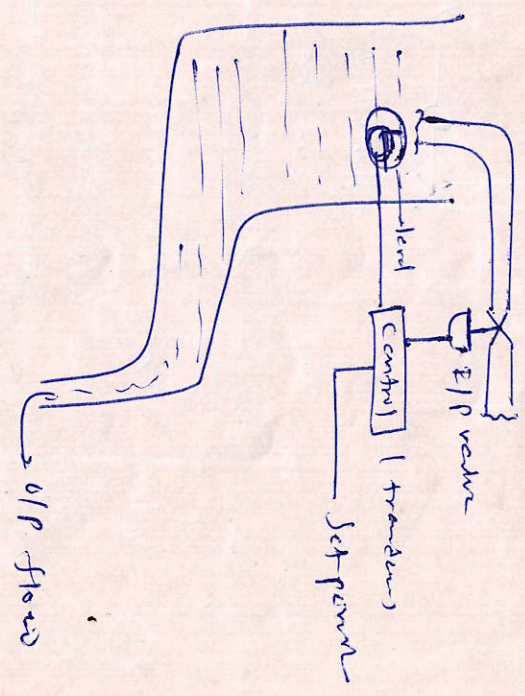⑦ Continuous Control => Fix: control the case of liquid level in a tank




Continuous Control System

* According to flow of liquid at o/p; transfer relayed the set point & when nature of I/P valve to maintain

as O/P flow is an unspecified flow & there is no control on O/P flow is called Continuous

Discrete Control System

Discrete state Control system

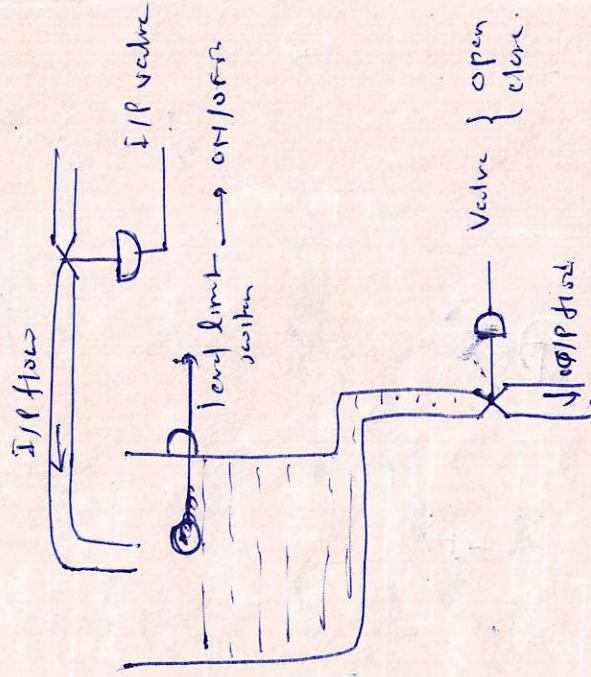

Here in this case we have some specific event sequence:

- 1 close the O/P valve
- 2 Open the I/P valve & let the tank to fill up to the desired level as indicated by level limit switch
- 3 close the I/P valve

so here three control valve


- 1 Level control by level limit switch — ON/OFF
- 2 I/P valve — open/close
- 3 O/P valve — open/close

& hence O/P flow is

specified & there is control on O/P flow is called Discrete state Control system

Composite Discrete & Control system

Batch filling by liquid

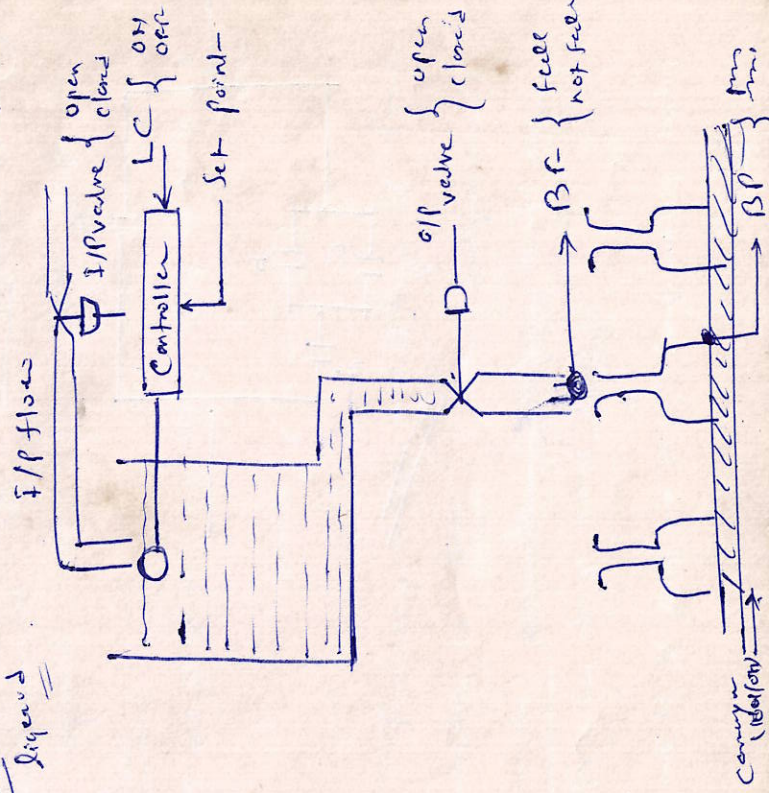


Composite = Combined of both
~~Ext~~ Centres + Discrete


Centres Control system is a part of ~~Centres~~ Discrete Control system.

Ladder Diagram

1. LD 100, LD 101, OR, ST0201

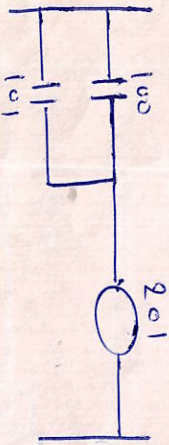

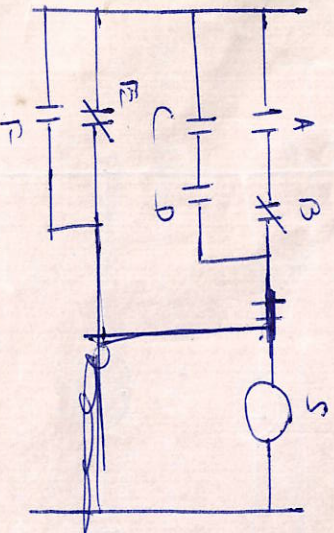
2. LDA, LDN B, AD, LDC, LDD, AND, OR, ST05, LDN E, LDR, ORS




Programming of PLC

- 01P channel = 00 to 07
- 01P channel = 08 to 15
- 01P Relays = 16 to 31
- Timers = 32 to 39

Ex

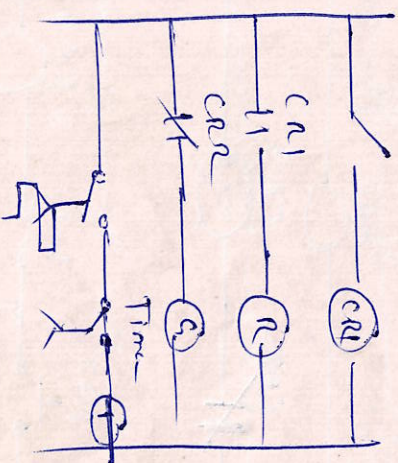

Ans

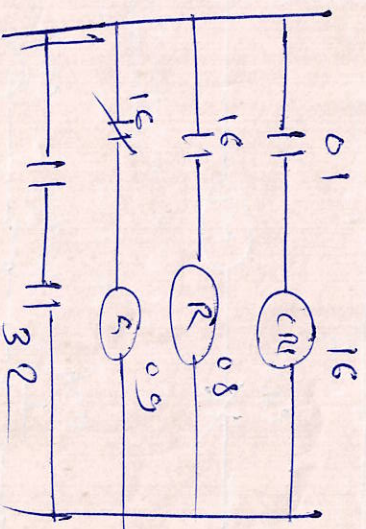

PLC

PC

PLC

① Hard disk

— Yes

NO

② Emulation

— (Direct)

Logical address decr

③ Signal Transmittion

— Directing

Industry

④ Language

— high level
function

Low level

⑤ Isolation

—

Yes

Isolation!
~~emulation~~